

# **BLG 212E Microprocessor Systems Homework 1**

Due: Tuesday, November 1, 2022

Lecturer: Ayşe Yilmazer CRN: 12629

**Fatih Baskın**

150210710

## Contents

<b>Problem 1</b>	<b>3</b>
a) Memory Map . . . . .	3
b) Chip Select Functions and Memory Circuit . . . . .	4
<b>Problem 2</b>	<b>5</b>
a) Memory Address Range . . . . .	5
b) Memory Circuit . . . . .	5



Chip Type	Chip Name	Starting Address(bin)	Ending Address(bin)	Address Range(hex)
2K8	2K8#1	0000 0000 0000 0000	0000 0111 1111 1111	\$0000 - \$07FF
2K8	2K8#2	0000 1000 0000 0000	0000 1111 1111 1111	\$0800 - \$0FFF
2K8	2K8#3	0001 0000 0000 0000	0001 0111 1111 1111	\$1000 - \$17FF
2K8	2K8#4	0001 1000 0000 0000	0001 1111 1111 1111	\$1800 - \$1FFF
2K8	2K8#5	0010 0000 0000 0000	0010 0111 1111 1111	\$2000 - \$27FF
2K8	2K8#6	0010 1000 0000 0000	0010 1111 1111 1111	\$2800 - \$2FFF
4K8	4K8#1	0011 0000 0000 0000	0011 1111 1111 1111	\$3000 - \$3FFF
16K8	16K8#1	0100 0000 0000 0000	0111 1111 1111 1111	\$4000 - \$7FFF

Table 1: Memory chips and their memory spans, red bits are used for chip selection.

## b) Chip Select Functions and Memory Circuit

The bits shown in red should be used in the chip selection process. When 0 signal arrives chip select, that chip is selected ( $\overline{CS_x}$ ), also address bit  $A_{15}$  is always 0 in address selection, so for the chip selection, address bits  $A_{14} - A_{11}$  can be used in the decoder, then the decoder output can be logical **AND**ed with  $\overline{A_{15}}$  since  $A_{15}$  was always 0 in chip selection. For the chip select, the output should be 0, so complementing the **AND** operation, effectively **NAND**ing should give 0 in the correct input combinations. Since **NAND**ing is effectively complementing **OR** gate's inputs, we can complement decoder outputs take  $A_{15}$  directly, zero signal would be provided in the correct input combinations. Decoder inputs are 4 bits,  $A_{14} - A_{11}$  and outputs are  $O_{15} - O_0$  (4 to 16 decoder).

- $\overline{CS_{2K8\#1}} = \overline{A_{15} \cdot O_0} = A_{15} + \bar{O}_0$
- $\overline{CS_{2K8\#2}} = \overline{A_{15} \cdot O_1} = A_{15} + \bar{O}_1$
- $\overline{CS_{2K8\#3}} = \overline{A_{15} \cdot O_2} = A_{15} + \bar{O}_2$
- $\overline{CS_{2K8\#4}} = \overline{A_{15} \cdot O_3} = A_{15} + \bar{O}_3$
- $\overline{CS_{2K8\#5}} = \overline{A_{15} \cdot O_4} = A_{15} + \bar{O}_4$
- $\overline{CS_{2K8\#6}} = \overline{A_{15} \cdot O_5} = A_{15} + \bar{O}_5$
- $\overline{CS_{4K8\#1}} = \overline{A_{15} \cdot (O_6 + O_7)} = A_{15} + (\bar{O}_6 \cdot \bar{O}_7)$
- $\overline{CS_{16K8\#1}} = \overline{A_{15} \cdot OR(O_{15} - O_8)} = A_{15} + (\bar{O}_8 \cdot \bar{O}_9 \cdot \bar{O}_{10} \cdot \bar{O}_{11} \cdot \bar{O}_{12} \cdot \bar{O}_{13} \cdot \bar{O}_{14} \cdot \bar{O}_{15})$

 


Figure 2: Memory circuit (Zoom in to see better, high resolution picture)

## Problem 2

In this problem, using 4K4  $\bar{R}/W$  chips, 16K8 memory should be implemented. Memory space should start from \$8000, there are 16 address bits and 8 data bits.

### a) Memory Address Range

Since chips are 4-bits wide, there should be 2 chips per same address range, those chips will be called "L" and "H", meaning the lowest significant half-byte and highest significant half-byte respectively. Since these chips are all 4Ks,  $2^{12} = 4K$  so 12 bits will be spared for address selection inside the chip, and the remaining 4 bits will be used for chip selection. This means using 4 to 16 decoder. Since each address range requires 2 chips and there are 4 address ranges ( $16K/4K = 4$ ) there will be 8 chips in total.

Chip Type	Chip Name	Starting Address(bin)	Ending Address(bin)	Address Range(hex)
4K4	4K4#1H & 4K4#1L	1000 0000 0000 0000	1000 1111 1111 1111	\$8000 - \$87FF
4K4	4K4#2H & 4K4#2L	1001 0000 0000 0000	1001 1111 1111 1111	\$9000 - \$97FF
4K4	4K4#3H & 4K4#3L	1010 0000 0000 0000	1010 1111 1111 1111	\$A000 - \$A7FF
4K4	4K4#4H & 4K4#4L	1011 0000 0000 0000	1011 1111 1111 1111	\$B000 - \$B7FF

Table 2: Memory chips and their memory spans, red bits are used for chip selection.

### b) Memory Circuit

 


Figure 3: Memory circuit (Zoom in to see better, high resolution picture)